

INSTRUCTIONS

1. Write name and RollNo in the space provided below and also on the answer book(s).
2. Printed, photocopied, phone, calculator etc. and exchange of any material is NOT allowed.
3. At the end of examination, return the question paper and answer book(s).
4. Solve questions serially in the answer script.

RollNo 

--	--	--	--	--	--	--	--

 Name: 

--

Question	1	2	3	4	5	Total
Points	2	3	5	10	10	30
Score						

1. (a) Write the behavioral statement for 3-input NAND gate using AND and NOT operator and assign it to output y. The gate has a delay of 2 time units. 2

--

2. (a) We have declared two sets of wires as follows: 3

```

wire [2:0] w1, w2;
wire [5:0] bundle;
    
```

Write a Verilog statement to create the bundle using most significant bit of w1 and least significant bit of w2.

--

3. (a) Does the following verilog code result in a sequential circuit or combinational circuit? Reason your answer as well. 5

```

module IdentifyCKT(input [1:0] in_data, input mask, output reg [1:0] out_data);
always @ (*)
begin
out_data[1] = in_data[1];
if (mask)
out_data[0] = 0;
end
endmodule
    
```

--

4. (a) Implement the behavioral verilog module called PrimeAndDiv in your simulator. The PrimeAndDiv module receives four inputs  $A_{3:0}$ , and two outputs, P and D. The input  $A_{3:0}$  represent a number from 0 to 15. Output P should be True, if the number is prime 10

(note that 0 and 1 are not prime, but, 2, 3, 4 and so on, are prime). Output D should be TRUE if the number is divisible by 3.

5. (a) Implement the structural Verilog module to compute the logic function  $F(A, B, C)$  in your simulator.

10

$$F(A, B, C) = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$